

Lab 5: Sensing Part 2

EECS 16B Spring 2024

Slides: links.eecs16b.org/lab5-slides


Administrivia

- **Continue working on the Midterm Lab report! It is due 3/6**
- The following two week are a buffer weeks (lab makeups) + time to study for midterm


For all forms, the lab section is meant to be your regular lab section!

Lab 5 Overview

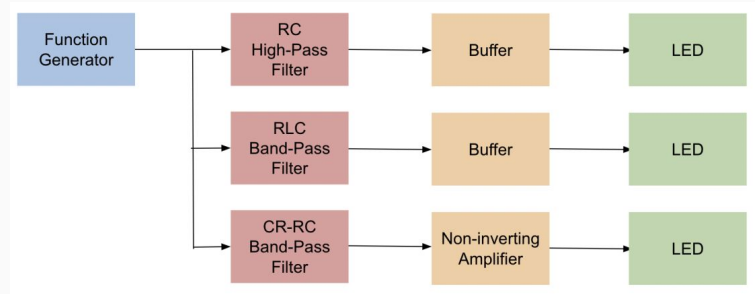- Re-tune your mic board
- Implement the following:
 - High Pass Filter (HPF)
 - RLC Band-Pass Filter
 - Cascading Bandpass Filter
- **Today's circuitry is entirely separate from the car!**
 - Use the spare breadboard at each station
 - RETURN THE OP-AMPS, LEDs, and INDUCTORS used for today's lab



Breadboard Reminder

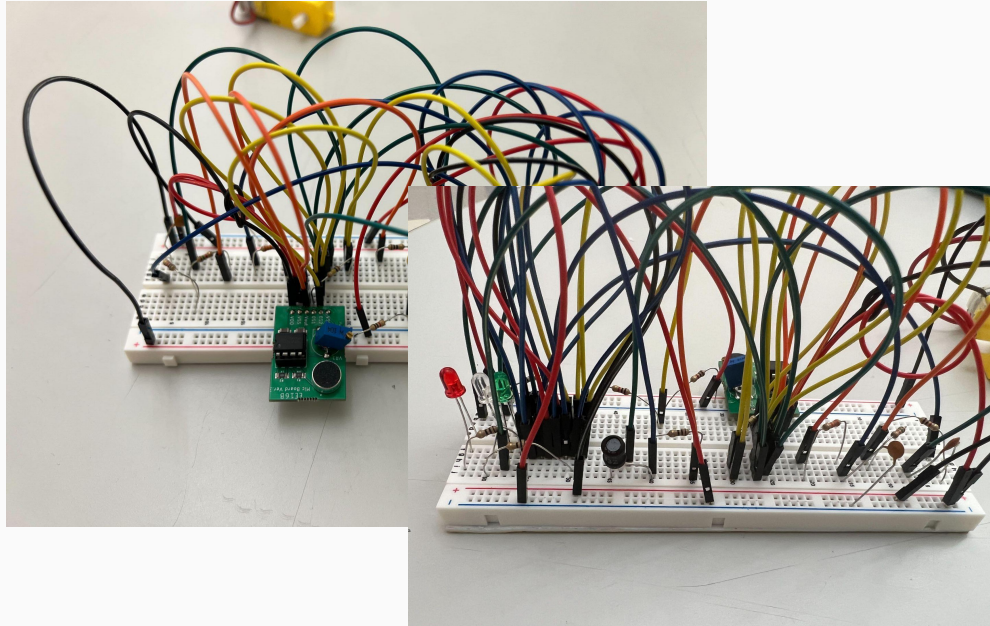

- **Messy Wiring**, and the use of excessive **Jumper Wires** make circuits exponentially more difficult to debug.
- This lab contains a lot of components, and require a lot of space. Plan how you will lay out your circuit wisely!

Filters

First Order Filters

- **Cutoff frequency** (f_c) is where signal has attenuated by 1/2 power (3dB)

- Recall:


$$P = IV = \frac{V^2}{R}$$
$$\frac{P}{2} = \frac{1}{2} \cdot \frac{V^2}{R} = \frac{1}{R} \left(\frac{V}{\sqrt{2}} \right)^2$$

- We can find the cutoff frequency by finding the frequency that causes the voltage to drop to $(1/\sqrt{2})V_0 \approx \mathbf{0.707V_0}$
- For RC circuits, the cutoff frequency is given by: $f_c = \frac{1}{2\pi RC}$ [Hz]

High-pass Filter Cutoff Derivation


High Pass Filter

Circuit Schematic

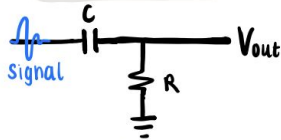

Think: the "gate" is higher.

High Pass Frequency Response

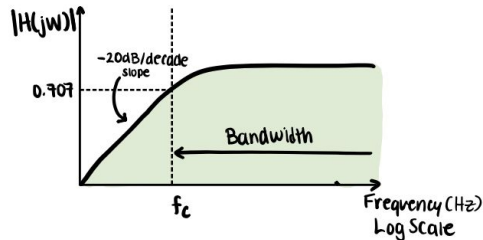

$$\hat{V}_{out} = \hat{V}_{in} \cdot \frac{Z_R}{Z_R + Z_C} = \hat{V}_{in} \frac{R}{\frac{1}{j\omega C} + R}$$

$$|H(j\omega)| = \frac{|\hat{V}_{out}|}{|\hat{V}_{in}|} = \frac{1}{\sqrt{2}} = \frac{\sqrt{R^2}}{\sqrt{\left(\frac{1}{\omega C}\right)^2 + R^2}}$$

$$\frac{1}{2} = \frac{R^2}{\left(\frac{1}{\omega C}\right)^2 + R^2}$$

$$\left(\frac{1}{\omega C}\right)^2 + R^2 = 2R^2$$

$$\left(\frac{1}{\omega C}\right)^2 = R^2$$

$$\omega = \frac{1}{RC} \quad \text{angular cutoff frequency}$$

$$f_c = \frac{1}{2\pi RC} \quad \text{cutoff frequency}$$

Conceptually: as $\omega \rightarrow \infty$, $|H(j\omega)| \rightarrow 1$
as $\omega \rightarrow 0$, $|H(j\omega)| \rightarrow 0$

New Component: Inductor




- Inductors MAY be polarized (to be consistent, assume the long leg is (+) and short leg is (-), and breadboard accordingly).
- These inductors are to be LOANED, make sure to return them once you are done with the lab / leave for the day!
- Do not cut their legs or bend them too much!

RLC Filters (make sure to return inductor)

- **Resonance Frequency:** The only frequency where the signal gets attenuated **OR** the only frequency where the signal passes through (depends on your filter implementation!)
- **Q factor:** The quality of the filter (is there a steep attenuation slope?), a higher Q factor -> higher quality filter.
- **Resonance Frequency:** $\omega = \sqrt{1/(LC)}$, $f = \omega/(2\pi)$,
- **Q Factor (only for RLC in series)** = $\omega L/R$ (ω = Resonance frequency)

Resonance Frequency Derivation

RLC Bandpass

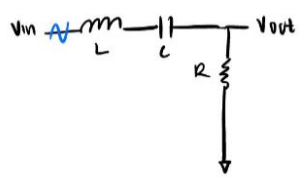

$$\begin{aligned}
 H(j\omega) &= \frac{v_{out}}{v_{in}} = \frac{z_R}{z_R + z_L + z_C} \\
 &= \frac{R}{\frac{1}{j\omega C} + j\omega L + R} \\
 &= \frac{1}{1 + j(\omega L - \frac{1}{\omega C})}
 \end{aligned}$$

Resonant Frequency \Rightarrow when $|H(j\omega)| = 1$

$$\begin{aligned}
 \Rightarrow \text{when } \omega L - \frac{1}{\omega C} &= 0 \\
 \Rightarrow \omega^2 L - \frac{1}{C} &= 0 \\
 \omega^2 &= \frac{1}{LC} \\
 \omega &= \sqrt{\frac{1}{LC}} \\
 \Rightarrow \text{resonant frequency } \omega_0 &= \sqrt{\frac{1}{LC}}
 \end{aligned}$$


Series Damping: $\alpha = \frac{R}{2L}$ (see lecture 3B)

Series Damping: $\alpha = \frac{R}{2L}$ (see lecture 3B)

poles: $-\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$


Q factor: $\frac{\omega_0 L}{R}$

Magnitude Response:

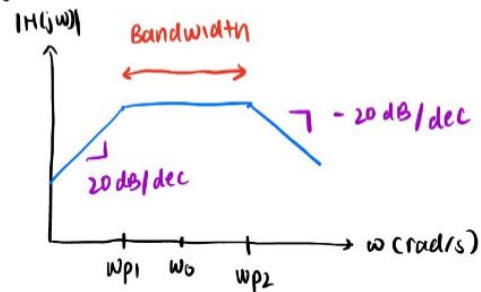

RC Band Pass


RC Bandpass

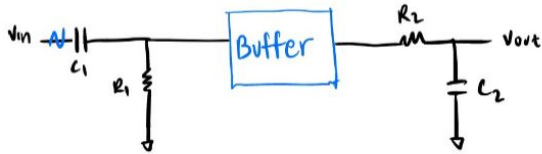

$$H(j\omega) = \frac{v_{out}}{v_{in}} = \frac{z_{R_1}}{z_{R_1} + z_{C_1}} \cdot \frac{z_{C_2}}{z_{R_2} + z_{C_2}} = \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} \cdot \frac{1}{1 + j\omega R_2 C_2}$$

poles: $\omega_{p1} = \frac{1}{R_1 C_1}$, $\omega_{p2} = \frac{1}{R_2 C_2}$

zeros: $\omega_z = 0$

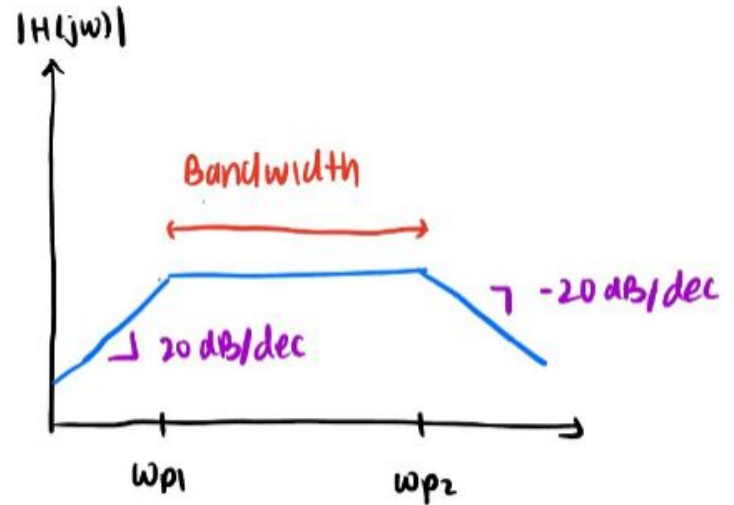


Debugging: Why aren't my LEDs lighting up?

- Make sure your filter(s) indeed does work using the function generator (sweep a range of frequencies, ones that should be attenuated, and ones that should pass through).
- Build a non-inverting amplifier
- DON'T USE WHITE LEDs

Review: Non-Inverting Amplifier Schematic

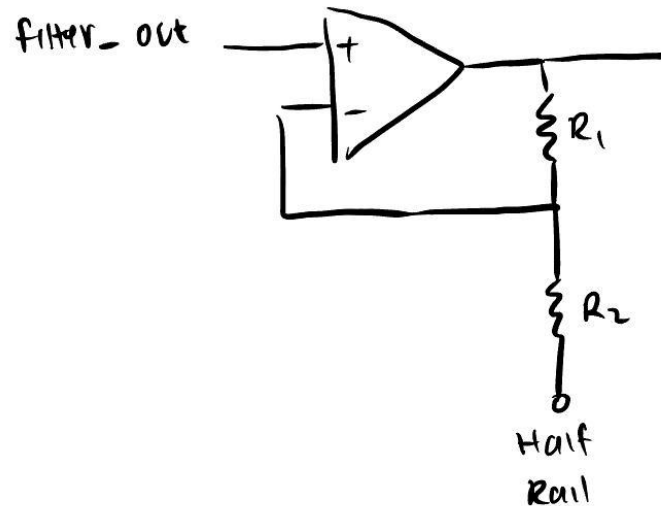* Buffer can be swapped for non-inverting amplifier!



$$\text{Gain} = 1 + \frac{R_1}{R_2}$$

* Choose reasonable ($1k\Omega >$) values for R_1, R_2 .

Important Forms/Links

- Help request form: <https://eecs16b.org/lab-help>
- Checkoff request form: <https://eecs16b.org/lab-checkoff>
- Slides: <links.eecs16b.org/lab5-slides>
- Anon Feedback: <https://eecs16b.org/lab-anon-feedback>
- Lab Grades error: <https://links.eecs16b.org/lab-checkoff-error>